
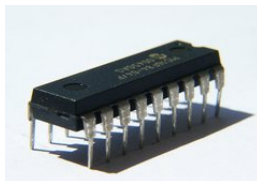


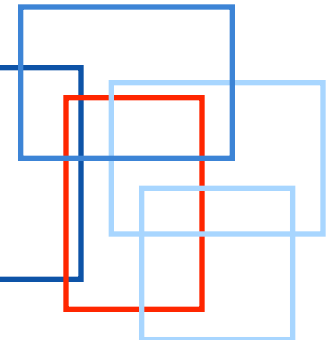

Circuitos Eléctricos II





**Ejemplos
Capítulo 11**



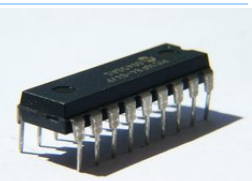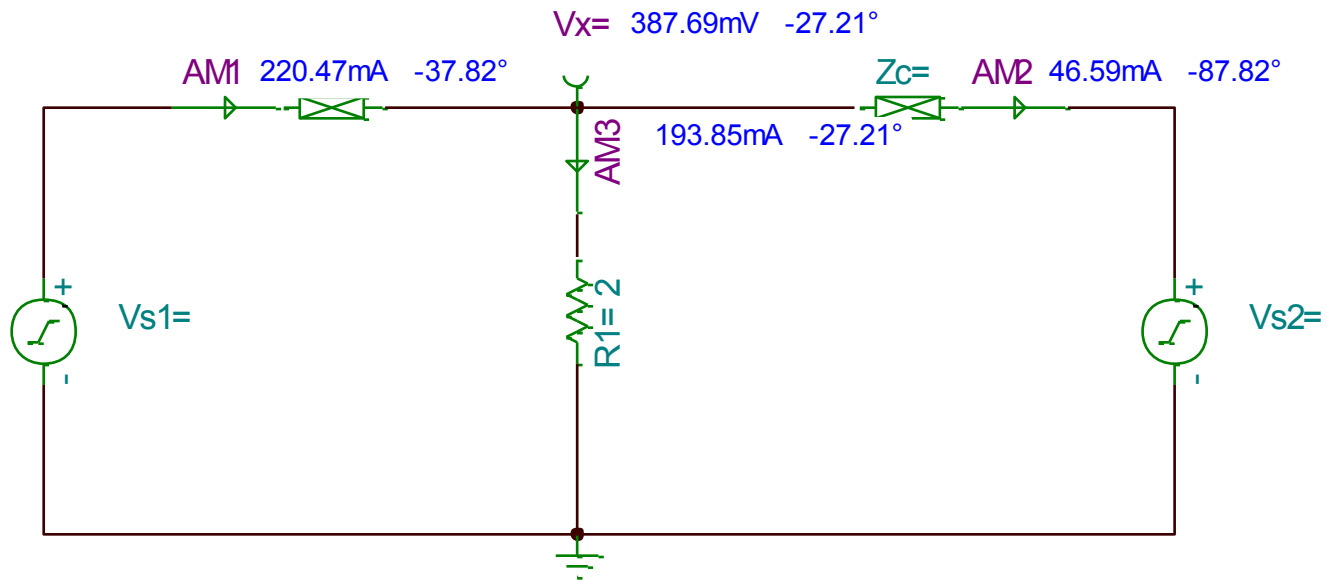Problema: "PRACTICE" 11.4 página 428

Calcule la potencia promedio de todos los elementos del circuito.



12. Calculate the average power generated by each source and the average power delivered to each impedance in the circuit of Fig. 11.30.



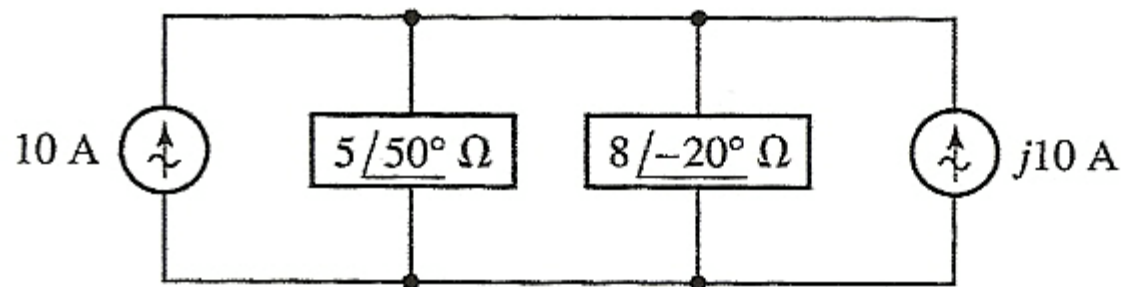


FIGURE 11.30

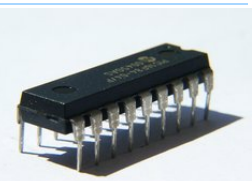

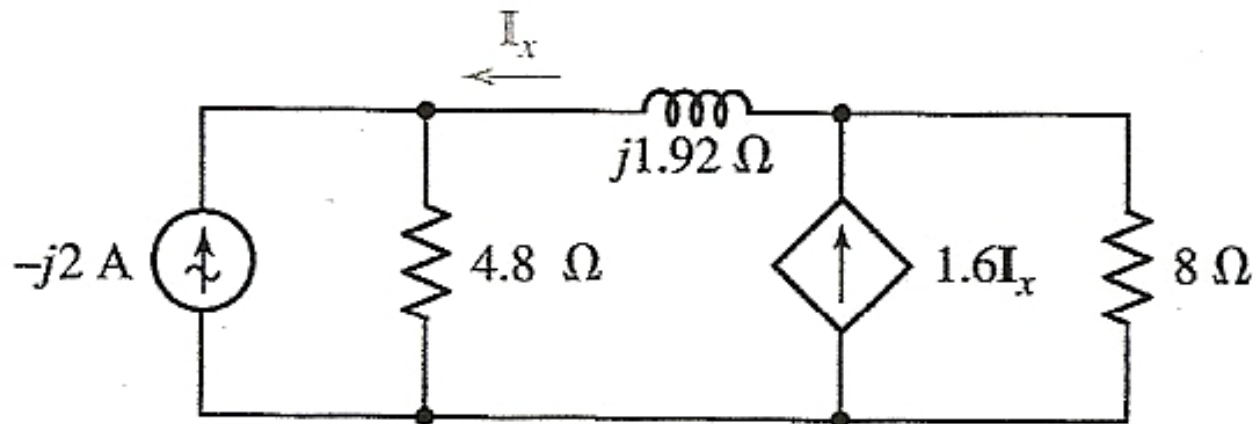19. Find the average power supplied by the dependent source of Fig. 11.35.



■ **FIGURE 11.35**



Ejemplo
Problema 11.45
Capítulo 11 página 454

45. A composite load consists of three loads connected in parallel. One draws 100 W at a PF of 0.92 lagging, another takes 250 W at a PF of 0.8 lagging, and the third requires 150 W at a unity PF. The parallel load is supplied by a source V_s in series with a $10\ \Omega$ resistor. The loads must all operate at 115 V rms. Determine (a) the rms current through the source; (b) the PF of the composite load.



Ejemplo
Problema 11.46
Capítulo 11 página 454

46. The load in Fig. 11.50 draws 10 kVA at $\text{PF} = 0.8$ lagging. If $|\mathbf{I}_L| = 40$ A rms, what must be the value of C to cause the source to operate at $\text{PF} = 0.9$ lagging?

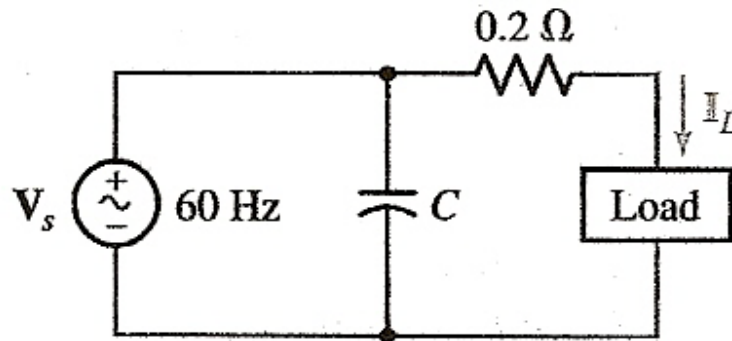


FIGURE 11.50



Ejemplo
Problema 11.48
Capítulo 11 página 454

48. Analyze the circuit of Fig. 11.52 to find the complex power absorbed by each of the five circuit elements.

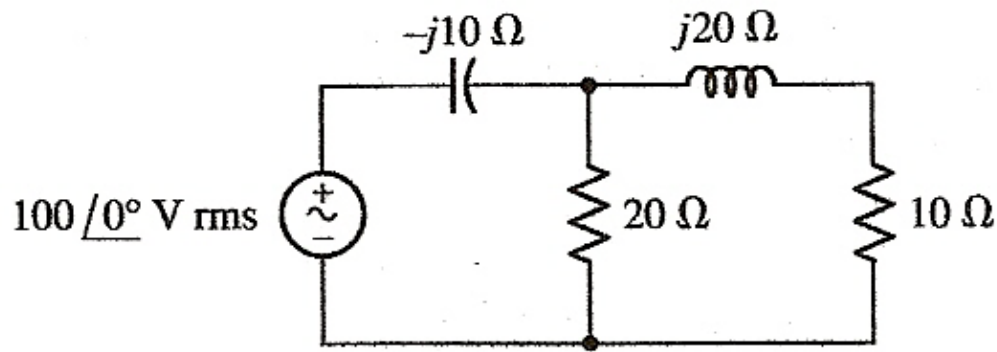


FIGURE 11.52



Ejemplo
Problema 11.49
Capítulo 11 página 455

49. Both sources shown in Fig. 11.53 are operating at the same frequency. Find the complex power generated by each source and the complex power absorbed by each passive circuit element.

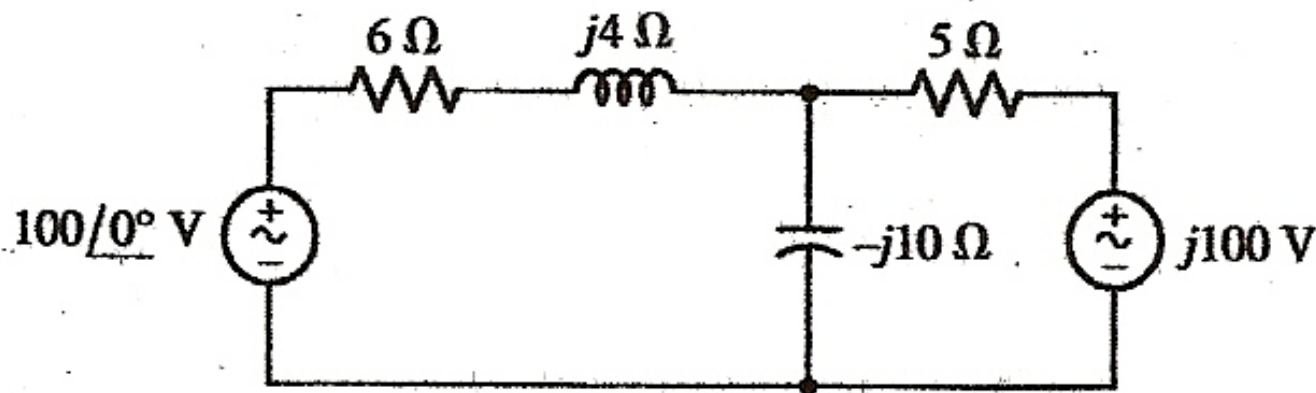


FIGURE 11.53



Ejemplo
Problema 11.51
Capítulo 11 página 455

51. A capacitive impedance, $Z_C = -j120\ \Omega$, is in parallel with a load Z_L . The parallel combination is supplied by a source, $V_s = 400/0^\circ\ \text{V rms}$, that generates a complex power of $1.6 + j0.5\ \text{kVA}$. Find the (a) complex power delivered to Z_L ; (b) PF of Z_L ; (c) PF of the source.



Ejemplo
Problema 11.52
Capítulo 11 página 455

52. A source of 230 V rms is supplying three loads in parallel: 1.2 kVA at a lagging PF of 0.8, 1.6 kVA at a lagging PF of 0.9, and 900 W at unity PF. Find (a) the amplitude of the source current; (b) the PF at which the source is operating; (c) the complex power being furnished by the source.

