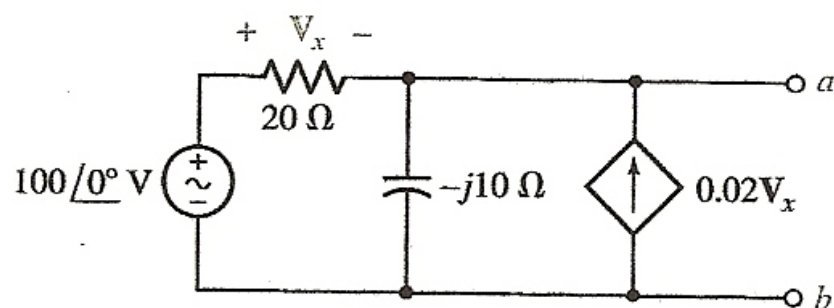


Circuitos Eléctricos II


Thévenin y Norton

Ejemplos

76. Find the frequency-domain Thévenin equivalent of the network shown in Fig. 10.75. Show the result as V_{th} in series with Z_{th} .



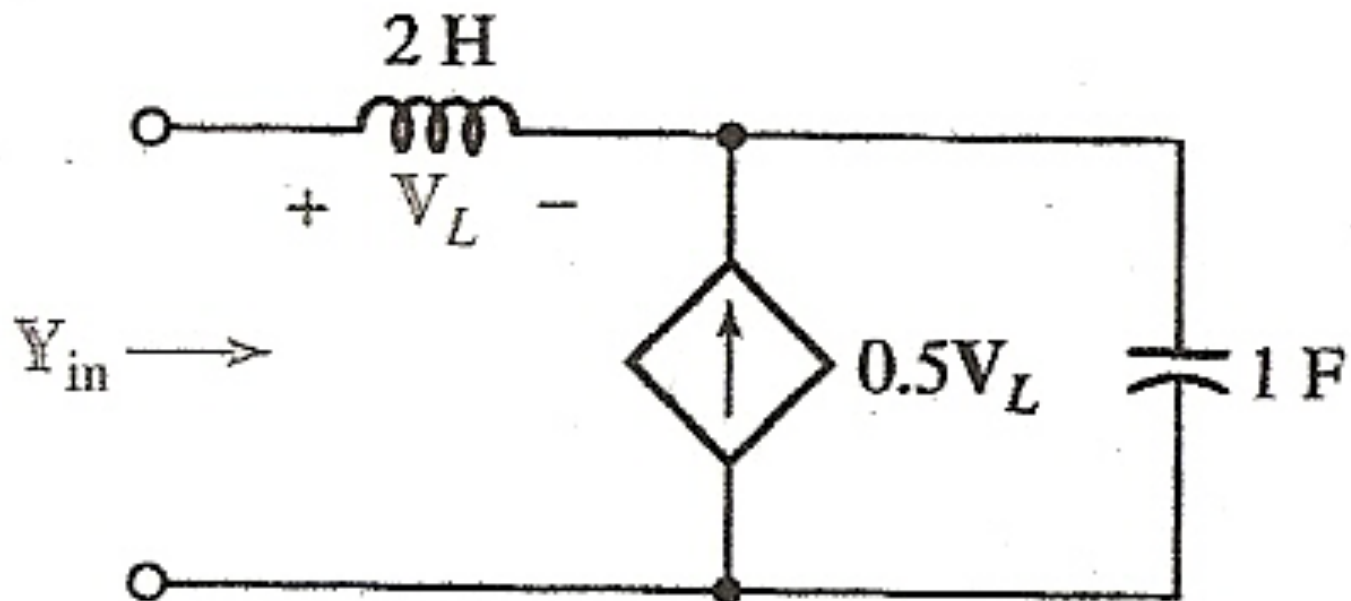77. Find the input admittance of the circuit shown in Fig. 10.76, and represent it as the parallel combination of a resistance R and an inductance L , giving values for R and L if $\omega = 1$ rad/s.



■ **FIGURE 10.76**

78. With reference to the circuit of Fig. 10.77, think superposition and find that part of $v_1(t)$ due to (a) the voltage source acting alone; (b) the current source acting alone.



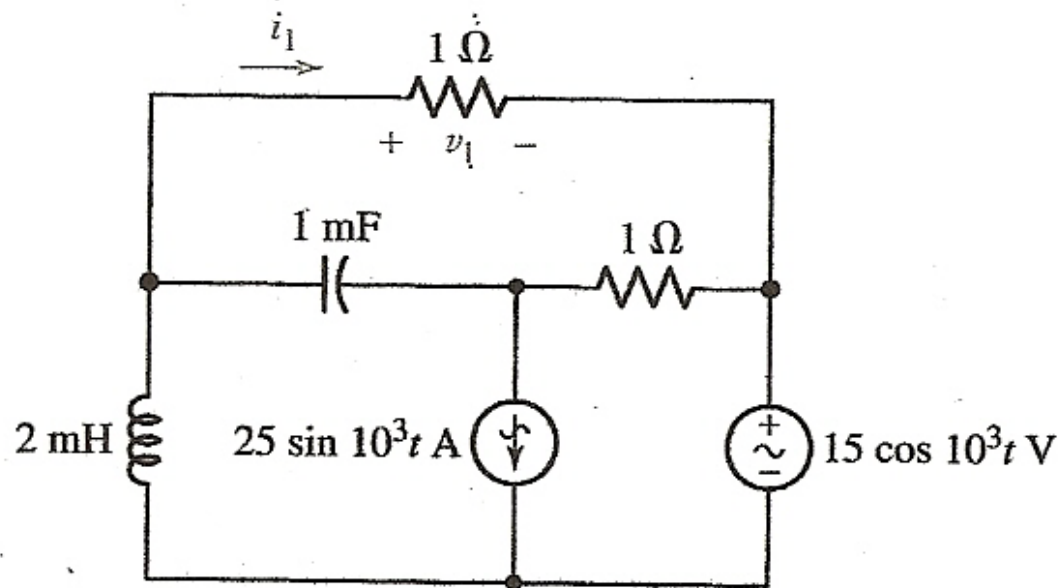


FIGURE 10.77

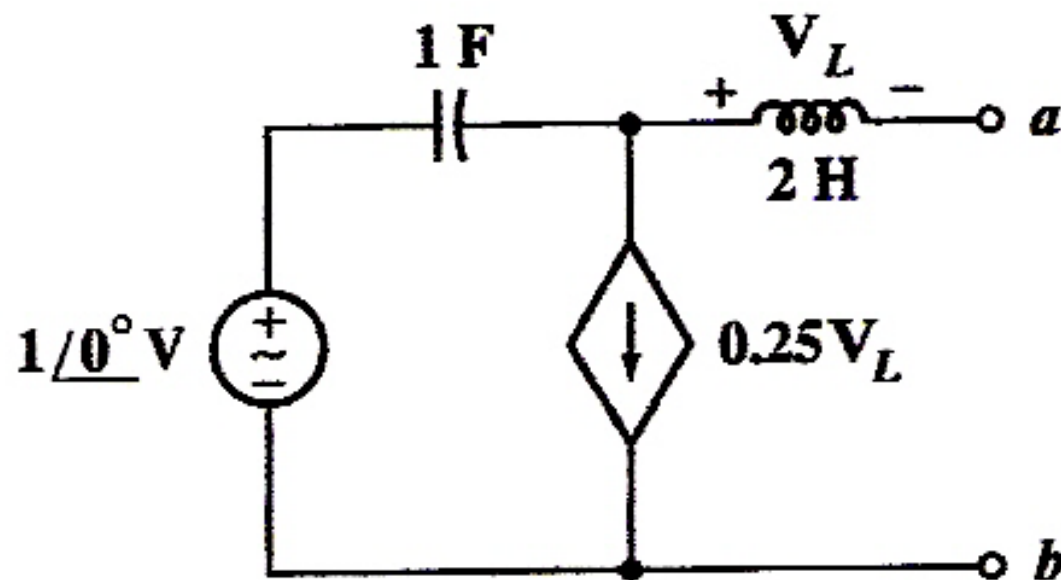Determine el equivalente de Thévenin entre las terminales a-b del circuito de la figura P2, con $\omega = 1 \text{ rad/s}$.



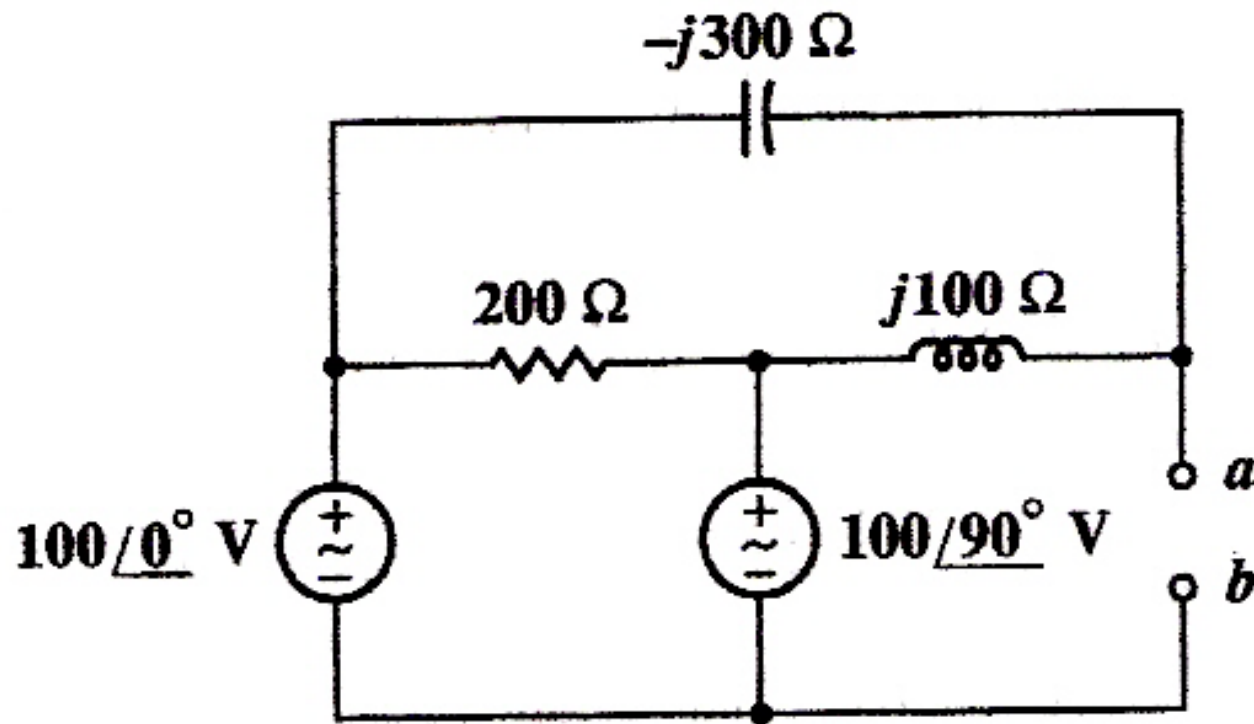Determine el equivalente de Thévenin en terminales a-b



Determine el equivalente de Thévenin entre las terminales a-b

